

Question 785

28-06
0.42-40%

In the circuit shown in figure 5, what is the current in the 8.00-Ohm resistor?

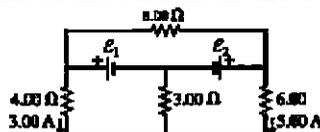


Figure 5

- (a) 11.25 A to the right
- (b) 3.38 A to the left
- (c) 11.25 A to the left
- (d) 2.25 A to the right
- (e) 2.25 A to the left

Question 786

28-06
0.27-23%

A number of 240-Ohms resistors are connected in parallel to a 120-V source. If the maximum current allowed in the circuit is 9 A, determine the largest number of resistors, which can be used in this circuit without exceeding the maximum current.

- (a) 9.
- (b) 25.
- (c) 36.
- (d) 18.
- (e) 34.

Question 787

28-06
0.44-35%

In figure 6, three identical light bulbs are connected to a battery. Which one of the following statements is CORRECT?

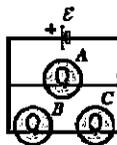


Figure 6

- (a) The smallest current passes through A.
- (b) The current through all resistors is the same.
- (c) The largest current passes through A.
- (d) The largest current passes through B.
- (e) The largest current passes through C.

28-7 The Ammeter and the Voltmeter

28-8 RC circuits

Question 788

28-08
0.48-50%

A capacitor in an RC circuit is charged to 85% of its maximum value in 2.4 s. What is the time constant of this circuit?

- (a) 2.4 s
- (b) 1.9 s
- (c) 1.3 s
- (d) 2.9 s
- (e) 0.9 s

28-08

Question 789

A 4.00 micro-F capacitor is charged to 24.0 V. Find the charge on the capacitor 4.00 milliseconds after it is connected across a 200-Ohm resistor.

- (a) 100 micro-C
 - (b) 0.647 micro-C
 - (c) 15.5 micro-C
 - (d) 2.45 micro-C
 - (e) 0.324 micro-C
-

28-08

0.32-28%

Question 790

Which one of the following statements is WRONG:

- (a) The emf of a battery is equal to the terminal voltage when there is no current passing through the battery.
 - (b) Two resistors connected in parallel have the same potential difference across them.
 - (c) Kirchhoff's rules are statements of conservation of charge and energy.
 - (d) A charged capacitor connected to a resistor will discharge faster when the resistance is increased.
 - (e) If the voltage is held constant across a resistor, the power dissipated in the resistor decreases when the resistance increases.
-

28-08

0.50-37%

Question 791

A certain capacitor (initially uncharged), is connected in series with a resistor and a battery. After, being charged for 10 ms the charge on the capacitor is half of its maximum value. What is the time constant (RC) of the circuit?

- (a) 2.24 milli-s
 - (b) 45.3 milli-s
 - (c) 59.2 milli-s
 - (d) 20.5 milli-s
 - (e) 14.4 milli-s
-

28-08

Question 792

How long will it take a charged capacitor of 50.0×10^{-6} F to lose 30% of its initial energy if allowed to discharge through a 40 Ohm resistor?

- (a) no enough information.
 - (b) 0.36×10^{-3} s.
 - (c) 0.18×10^{-3} s
 - (d) 0.02×10^{-3} s.
 - (e) Infinity.
-

28-08

Question 793

The capacitor in figure (1) is initially charged to 50 V and then the switch is closed. What charge flows out of the capacitor during the first minute after the switch was closed?

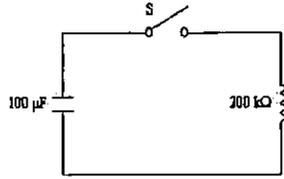


Figure 1

- (a) 3.6 mC.
- (b) 4.8 mC.
- (c) 0.3 mC.
- (d) 1.4 mC.
- (e) 1.7 mC.

28-08

Question 794

At $t=0$, a 2.0×10^{-6} Farad capacitor is connected in series to a 20-V battery and a 2.0×10^6 Ohm resistor. How long does it take for the potential difference across the capacitor to be 12 V?

- (a) 3.7 s.
- (b) 2.0 s.
- (c) 2.8 s.
- (d) 0.6 s.
- (e) 1.2 s.

28-08

Question 795

0.39-50%

A certain capacitor, in series with a 720-ohm resistor, is being charged. At the end of 10 milliseconds, its charge is 50 % of the maximum charge. The capacitance is:

- (a) 20 micro-Farad
- (b) 14 micro-Farad
- (c) 10 micro-Farad
- (d) 7.2 micro-Farad
- (e) 9.6 micro-Farad

28-08

Question 796

0.37-27%

In the circuit shown in figure 3, the capacitor was initially uncharged. At time $t = 0$, switch S is closed. If T denotes the time constant, the current through the 3-ohm resistor at $t = T/10$ is

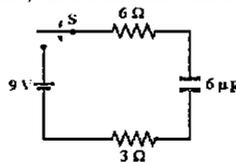


Figure 3

- (a) zero.
- (b) 0.90 A.
- (c) 1.5 A.
- (d) 2.5 A.
- (e) 3.0 A.

Question 79728-08
0.40-70%

A resistor $R = 30 \times 10^6 \text{ Ohm}$ is connected in series with a capacitor $C = 3.0 \text{ micro-F}$ and a 21-Volt battery for long time. The battery was removed, then R and C are connected in a loop. What is the energy stored in the capacitor C after one minute?

- (a) 47 micro-J.
 - (b) 11 micro-J.
 - (c) 204 micro-J.
 - (d) 24 micro-J.
 - (e) 174 micro-J.
-

Question 79828-08
0.57-41%

A capacitor, initially uncharged in a single-loop RC circuit, is charged to 85% of its final potential difference in 2.4 s. What is its time constant in seconds?

- (a) 2.8
 - (b) 1.5
 - (c) zero
 - (d) 1.7
 - (e) 1.3
-

Question 79928-08
0.53-45%

A 1-micro-Farad uncharged capacitor and a 3000-ohm resistor are connected in series, and then (at time $t = 0$) a 6-V potential difference is applied across them. Find the time at which the voltage on the capacitor is 3.8 V.

- (a) 8.0 ms
 - (b) 15 ms
 - (c) 1.5 ms
 - (d) 3.0 ms
 - (e) 12 ms
-

Question 80028-08
0.24-64%

A capacitor of capacitance C is discharging through a resistor of resistance R . In terms of RC , when will the energy stored in the capacitor reduce to one fifth of its initial value?

- (a) 0.70 RC .
 - (b) 1.20 RC .
 - (c) 0.55 RC .
 - (d) 0.80 RC .
 - (e) 0.35 RC .
-

Question 80128-08
0.61-53%

A 5.0-micro-F capacitor is fully charged by connecting it to a 12-V battery. After disconnecting the battery, it was allowed for capacitor to discharge through a simple RC circuit, with a time constant of 4.0 s. What is the charge on the capacitor after one time constant has elapsed?

- (a) $2.2 \times 10^{-5} \text{ C}$
 - (b) $3.8 \times 10^{-5} \text{ C}$
 - (c) $1.2 \times 10^{-5} \text{ C}$
 - (d) $7.4 \times 10^{-5} \text{ C}$
 - (e) $5.5 \times 10^{-5} \text{ C}$
-